

CIRCUITS (1)

solved exams & examples.

Contents:

1: exams (2008 final + midterm 2010/2011)

2: solved examples (3phase + resonance)

3: solved examples (impedance)

4: a circuit analysis solved with all methods

2.5 L.E.

First

Exams (2008 final+midterm2010/2011)

- 1- Use the principle of superposition to find i_1 and i_2 in the circuit shown in fig.(1). Then, determine which sources are generating power.

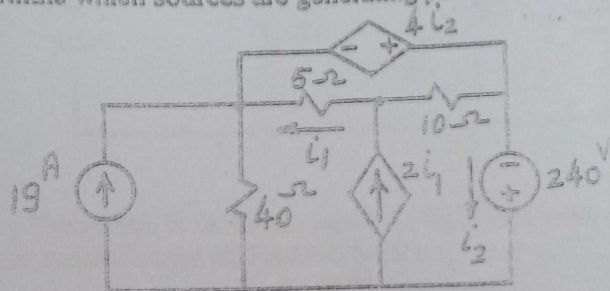


Fig.(1)

(15 marks)

- 2- For the circuit shown in fig.(2):

- find the value of R that enables the circuit to deliver maximum power to the terminals a and b .
- Find the maximum power delivered to R .
- When R is adjusted for maximum power transfer, how much power is the 100 V source delivering to the circuit?

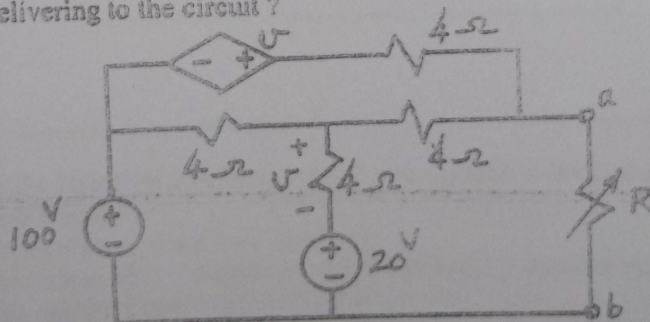


Fig.(2)

(15 marks)

- 3- The frequency of the sinusoidal current source shown in fig.(3) is adjusted for unity power factor resonance. Calculate:

- The resonant frequency ω_0 .
- The quality factor of the circuit.
- The amplitude of $v(t)$ when $i_s(t) = 50 \sin \omega_0 t$ mA.


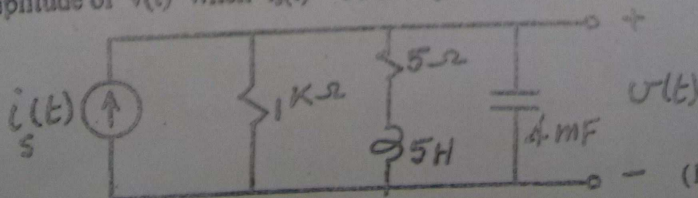


Fig.(3)


(15 marks)

4- a) The switch in the circuit shown in fig.(4) has been closed for a long time before opening at $t = 0$. Find:

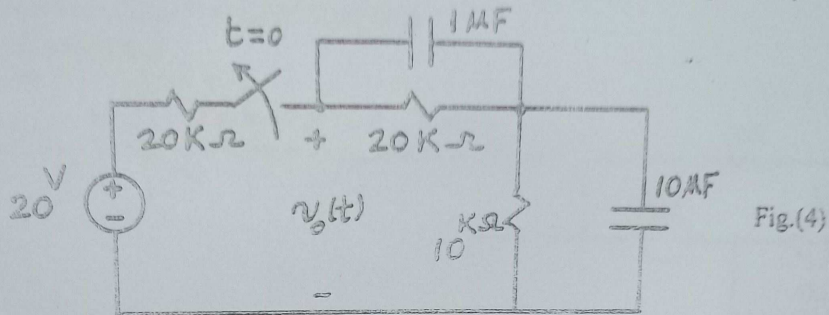- $v_o(t)$ for $t \geq 0$.
- The initial energy stored in capacitors at $t = 0$.
- The energy stored in capacitors after the switch has been opened by 50 m sec.



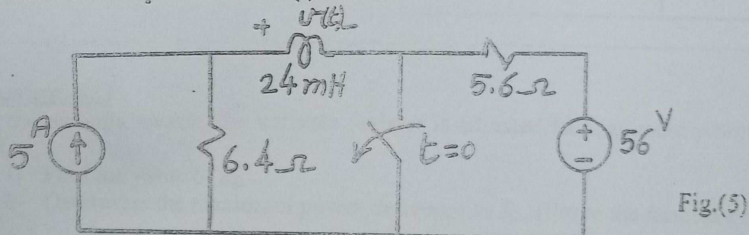
b) The switch in the circuit shown in fig.(5) has been closed for a long time. At $t = 0$, the switch is opened. Find $v(t)$ for $t \geq 0$.



(15 marks)

5- For the balanced 3-phase system shown in fig.(6), determine:

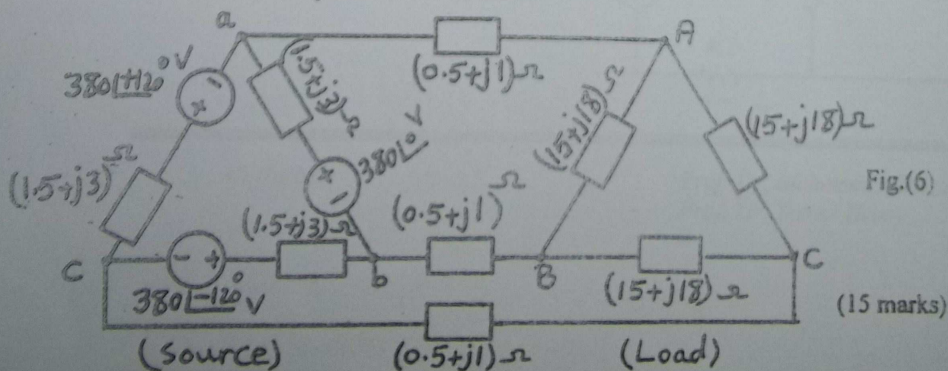- line currents.
- line voltages at the load terminals.
- the values of Δ -connected capacitors bank, connected at the load terminals in order to raise the power factor to 0.95.






Answer the following Questions

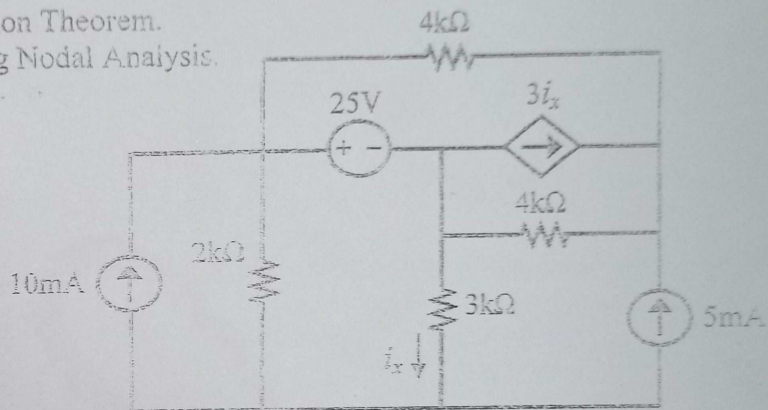Question (1)

For the circuit shown,


- 1- Find i_x using Superposition Theorem.
- 2- Verify your answer using Nodal Analysis.



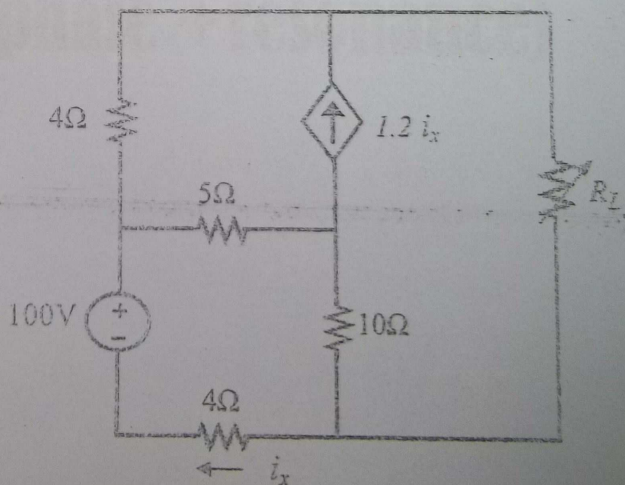Question (2)

For the network shown, the variable resistor is adjusted for maximum power transfer to R_L .

- 1- Find the value of R_L .
- 2- Determine the maximum power delivered to R_L . (Prove the formula used)



Second


Solved examples (3phase +resonance)

Example 1 Consider the circuit of Fig. 1.

(a) Find the resonant frequency ω_0 and the half-power frequencies ω_1, ω_2 .

(b) Calculate the bandwidth and quality factor.

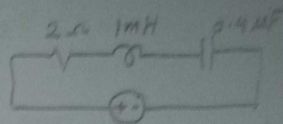(c) Determine the amplitude of current at ω_0, ω_1 and ω_2 .



$$v(t) = 20 \sin \omega t$$

Fig. 1

Solution

(a) The resonant frequency is

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-3} \times 0.4 \times 10^{-6}}} = 50 \times 10^3 \text{ r/s} = 50 \text{ K.r/s.}$$

The half-power frequencies are:

$$\omega_{1/2} = \mp \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \omega_0^2}$$

$$\therefore \omega_{1/2} = \mp \frac{2}{2 \times 1 \times 10^{-3}} + \sqrt{\left(\frac{2}{2 \times 1 \times 10^{-3}}\right)^2 + (50 \times 10^3)^2}$$

$$\therefore \omega_1 = 49009.99 \text{ r/s}, \quad \omega_2 = 51009.99 \text{ r/s.}$$

(b) The bandwidth is

$$\beta = \omega_2 - \omega_1 = 2000 \text{ r/s}$$

$$(\text{or, } \beta = \frac{R}{L} = \frac{2}{1 \times 10^{-3}} = 2000 \text{ r/s}).$$

\therefore The quality factor is

$$Q = \frac{\omega_0}{\beta} = \frac{50 \times 10^3}{2000} = 25 \quad (\text{dimensionless}).$$

$$(\text{or, } Q = \frac{\omega_0 L}{R} = \frac{50 \times 10^3 \times 1 \times 10^{-3}}{2} = 25).$$

Note that, since $Q > 10$, this is a high-Q circuit and we can calculate the half-power frequencies as:

$$\omega_{1/2} \approx \omega_0 \mp \frac{\beta}{2} = 50 \times 10^3 \mp \frac{2000}{2} = 50 \times 10^3 \mp 1 \times 10^3$$


$$\therefore \omega_1 \approx 49 \times 10^3, \quad \omega_2 \approx 51 \times 10^3 \text{ r/s.}$$

(c) since $I_p = \frac{V_{\max}}{R}$, at ω_0 ,

$$\therefore I_p = \frac{20}{2} = 10 \text{ A}$$


At ω_1 , or, ω_2 :
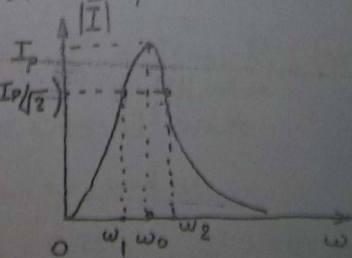
$$I(\omega_1) = I(\omega_2) = \frac{I_p}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.071 \text{ A}$$



Example 2 In the parallel RLC circuit of Fig. 2, find:

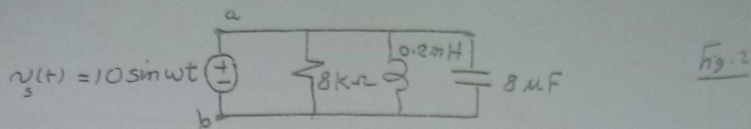- (a) ω_0 and Q . (b) ω_1 and ω_2 .
 (c) The power dissipated at ω_0 , ω_1 and ω_2 .



Solution

$$(a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.2 \times 10^{-3} \times 8 \times 10^{-6}}} = 25 \times 10^3 \text{ r/s.}$$

The bandwidth is $\beta = \frac{1}{RC}$, and the quality factor is

$$Q = \frac{\omega_0}{\beta} = \omega_0 RC \quad \therefore \beta = \frac{1}{8 \times 10^3 \times 8 \times 10^{-6}} = 15.625 \text{ r/s}$$

$$\therefore Q = 25 \times 10^3 \times 8 \times 10^3 \times 8 \times 10^{-6} = 1600$$

(b) since $Q > 10$, we can regard this circuit as a high- Q circuit. Therefore, the half power frequencies are approximately given by:

$$\omega_{1/2} = \omega_0 \mp \frac{\beta}{2} = 25 \times 10^3 \mp \frac{15.625}{2}$$

$$\therefore \omega_1 \approx 24.992 \times 10^3 \text{ r/s}, \quad \omega_2 \approx 25.008 \times 10^3 \text{ r/s.}$$

(c) At $\omega = \omega_0$, the circuit is pure resistive, i.e.,

$$\bar{Z}_{ab} = R = 8 \times 10^3 \Omega \quad (\text{see Fig. 3}).$$

$$\therefore i(\omega_0) = \frac{10}{8 \times 10^3} \sin \omega_0 t$$

$$\therefore i(\omega_0) = 1.25 \times 10^{-3} \sin(25 \times 10^3 t)$$

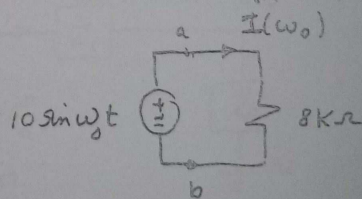


Fig. 3


Note that the entire current flows through the $8 \text{ k}\Omega$ resistor.

\therefore The power dissipated at ω_0 is $P_0 = I(\omega_0)^2 R$, (Watt).

$$\therefore P_{\omega_0} = \left(\frac{1.25 \times 10^{-3}}{\sqrt{2}} \right)^2 \times 8 \times 10^3 = 6.25 \times 10^{-3} \text{ Watt.}$$

At the half-power frequencies ω_1 and ω_2 :
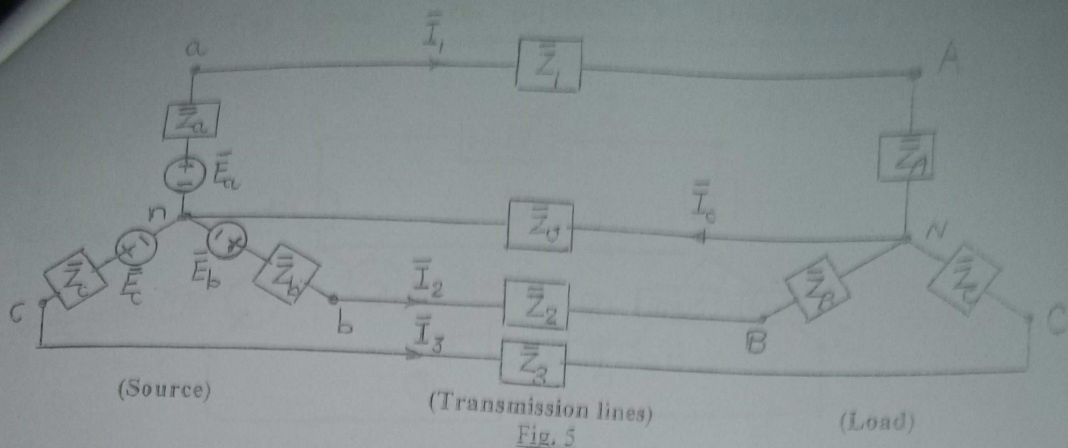
$$P_{\omega_1} = P_{\omega_2} = \frac{1}{2} P_{\omega_0} = \frac{1}{2} \times 6.25 \times 10^{-3} = 3.125 \times 10^{-3} \text{ W}$$



- (a) What are the conditions for the system to be balanced?
 (b) Mention the importance of phase sequence in 3-phase power distribution.
 (c) Consider the case of balanced 3-phase source of negligible internal impedance; with $\bar{E}_a = 100 \angle 0^\circ$ V, and abc phase sequence. Given that $\bar{Z}_1 = \bar{Z}_2 = \bar{Z}_3 = 1 + j2 \Omega$, and $\bar{Z}_0 = 0$. Calculate the line currents and total complex power delivered to each of the following loads:
 (i) Balanced load with $\bar{Z}_A = \bar{Z}_B = \bar{Z}_C = 9 + j8 \Omega$.
 (ii) Unbalanced load with $\bar{Z}_A = 15 \Omega$, $\bar{Z}_B = 10 + j5 \Omega$, and $\bar{Z}_C = 6 - j8 \Omega$.

Solution: (i) From the given data, the whole system is balanced.


Consequently, we use the per-phase equivalent circuit:

$$\bar{I}_1 = \frac{\bar{E}_a}{\bar{Z}_1 + \bar{Z}_A} = \frac{100 \angle 0^\circ}{1 + j2 + 9 + j8}$$

$$\therefore \bar{I}_1 = \frac{10}{\sqrt{2}} \angle -45^\circ$$

$$\therefore \bar{I}_2 = \frac{10}{\sqrt{2}} \angle -165^\circ$$
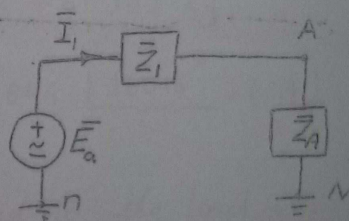
$$\therefore \bar{I}_3 = \frac{10}{\sqrt{2}} \angle 75^\circ$$



The total complex power delivered to the load is:

$$\bar{S}_l = 3 \bar{I}_1^2 \bar{Z}_A = 3 \left(\frac{10}{\sqrt{2}} \right)^2 (9 + j8)$$


$$\therefore \boxed{\bar{S}_l = 1350 + j120} \text{ (VA)}$$

(N.B.)

$$\bar{I}_0 = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 0$$

(page 4)

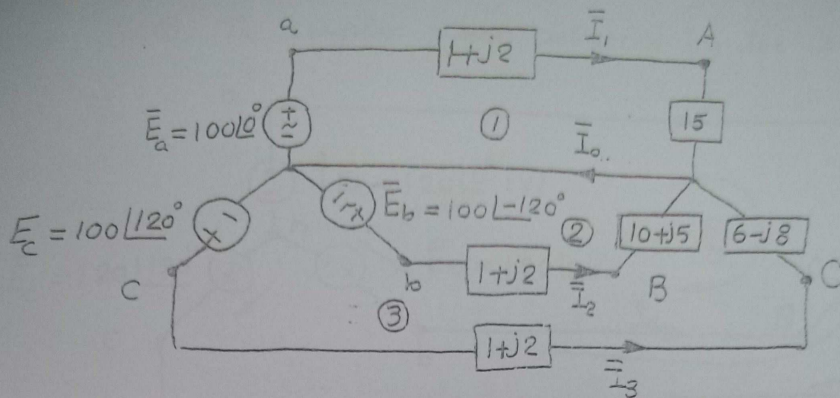(iv) In this case, the system is unbalanced, as shown below



Apply KVL around each of the three meshes :

Mesh ① : $\bar{E}_a = \bar{I}_1 (1+j2 + 15) = (16+j2) \bar{I}_1 = 100 \angle 0^\circ$

$$\therefore \bar{I}_1 = \frac{100 \angle 0^\circ}{(16+j2)} = 6.226 \angle -7.125^\circ, (A)$$

Mesh ② : $\bar{E}_b = 100 \angle -120^\circ = (1+j2 + 10+j5) \bar{I}_2$

$$\therefore \bar{I}_2 = \frac{100 \angle -120^\circ}{(11+j7)} = 7.67 \angle -152.47^\circ (A)$$

Mesh ③ : $\bar{E}_c = 100 \angle 120^\circ = (1+j2 + 6-j8) \bar{I}_3$

$$\therefore \bar{I}_3 = \frac{100 \angle 120^\circ}{(7-j6)} = 10.846 \angle 160.6^\circ (A)$$

The total complex power delivered to the load is :

$$\begin{aligned} \bar{S}_l &= \bar{I}_1^2 \bar{Z}_A + \bar{I}_2^2 \bar{Z}_B + \bar{I}_3^2 \bar{Z}_C \\ &= (6.226)^2 (15) + (7.67)^2 (10+j5) + (10.846)^2 (6-j8) \end{aligned}$$


$$\therefore \bar{S}_l = 1874.9 - j352.75 (VA)$$

N.B., $\bar{I}_o = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 \neq 0$

(page 5)

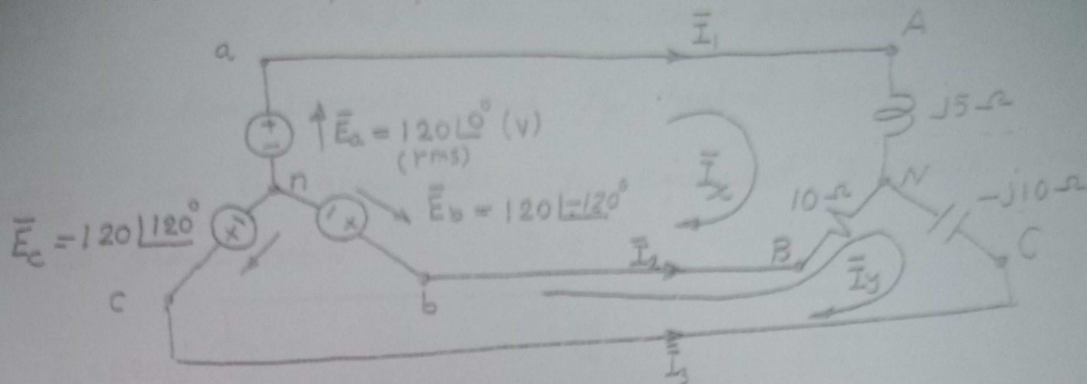Example (4)
Find

- The line currents.
- The complex power absorbed by the load.
- The complex power delivered by the source.



Solution

Let \bar{I}_x and \bar{I}_y be the 2-mesh currents

Mesh x: $(\bar{E}_a - \bar{E}_b) = (10 + j5)\bar{I}_x - 10\bar{I}_y = 120\angle 0^\circ - 120\angle -120^\circ$... ①

Note that: $(\bar{E}_a - \bar{E}_b) = \bar{E}_{ab} = \sqrt{3} \bar{E}_a \angle 30^\circ = \text{line voltage}$

Mesh y: $(\bar{E}_b - \bar{E}_c) = -10\bar{I}_x + (10 - j10)\bar{I}_y = 120\angle -120^\circ - 120\angle 120^\circ$... ②

Note that: $(\bar{E}_b - \bar{E}_c) = \sqrt{3} \bar{E}_b \angle 30^\circ = \text{line voltage}$

Solving ① and ②

$$\bar{I}_x = 56.78 \angle 0^\circ, \quad \bar{I}_y = 42.75 \angle 25^\circ$$

Therefore, the 3 line currents are:

$\bar{I}_1 = \bar{I}_x = 56.78 \angle 0^\circ$, $\bar{I}_2 = \bar{I}_y - \bar{I}_x = 25.46 \angle 135^\circ$, and

$\bar{I}_3 = -\bar{I}_y = -42.75 \angle 25^\circ = 42.75 \angle -155^\circ$ (A)

$\bar{S}_{\text{load}} = (56.78)^2(j5) + (25.46)^2(10) + (42.75)^2(-j10)$
 $\therefore \bar{S}_l = 6480 - j2156 \text{ (VA)}$ $\therefore \bar{S}_{\text{source}} = \bar{S}_l$


$\bar{S}_{\text{source}} = \sum \bar{E}_j \bar{I}_j^* = (120\angle 0^\circ)(56.78\angle 0^\circ) + (120\angle -120^\circ)(25.46\angle -135^\circ) + (120\angle 120^\circ)(42.75\angle 155^\circ) = 6480 - j2156 = \bar{S}_l$

Check:

A 3-phase, 4-wire, 380 V source is connected to an unbalanced load having phase impedances of: $\bar{Z}_A = 8 + j6 \Omega$, $\bar{Z}_B = 8 - j6 \Omega$, and $\bar{Z}_C = 5 \Omega$. The impedance of the neutral wire is $\bar{Z}_0 = 0.5 + j1 \Omega$. The phase sequence is abc.

Find the line currents and the neutral current.

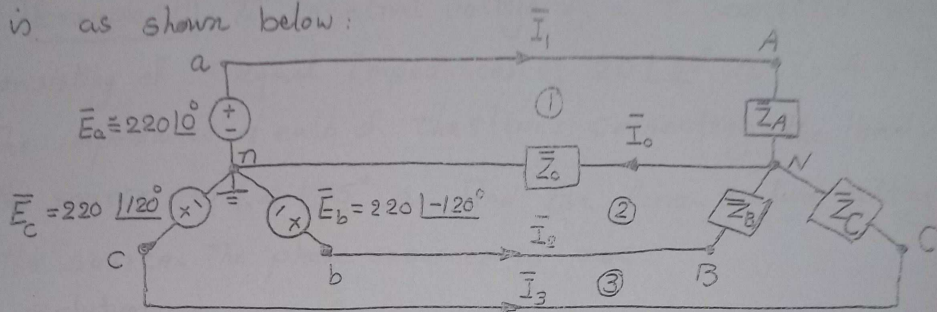Solution From the given data, the equivalent 3-phase circuit is as shown below:



Note that, the given 380 V is the effective (rms) value of line-to-line voltage of the source. Hence, the corresponding value of phase voltage is $\frac{380}{\sqrt{3}} \cong 220 \text{ V}$.

Using mesh analysis, the 3-mesh equations are:

$$220\angle 0^\circ = \bar{Z}_A \bar{I}_1 + \bar{Z}_0 \bar{I}_0 \quad (1)$$

$$220\angle -120^\circ = \bar{Z}_B \bar{I}_2 + \bar{Z}_0 \bar{I}_0 \quad (2)$$

$$220\angle 120^\circ = \bar{Z}_C \bar{I}_3 + \bar{Z}_0 \bar{I}_0 \quad (3)$$

$$\text{With } \bar{I}_0 = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 \quad (4)$$

Solving the 4 equations, yields:

$$\bar{I}_1 = 22.1 \angle -36.3^\circ \text{ A}, \quad \bar{I}_2 = 21.86 \angle 82.4^\circ \text{ A},$$

$$\bar{I}_3 = 43.45 \angle 119.4^\circ \text{ A}, \quad \text{and } \bar{I}_0 = 3.12 \angle 104^\circ \text{ A}.$$

Important note: Since $\bar{I}_0 \neq 0$, $\therefore \bar{V}_N - \bar{V}_n = \bar{Z}_0 \bar{I}_0$. Therefore, if $\bar{V}_n = 0$ (as reference), $\bar{V}_N = \bar{Z}_0 \bar{I}_0 = -3.14 + j0.76$. (page 7)

(3-phase system)

N.B. When we speak of a 3-phase system, the terms voltage, current and power are understood to mean line-to-line voltage, line current and total 3-phase power, respectively.

Example (1), The terminal voltage of a Y-connected load consisting of 3 equal impedances of $20 \angle 30^\circ \Omega$ is 4.4 kV. The impedance of each of the 3 lines connecting the load to the source is $1.4 \angle 75^\circ \Omega$. Find the line-to-line voltage at the source. The phase sequence is abc.

Solution:

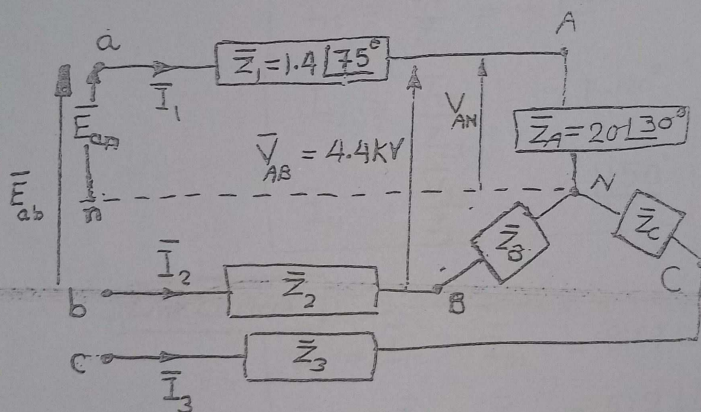


Fig. 1 : Given 3-phase system.

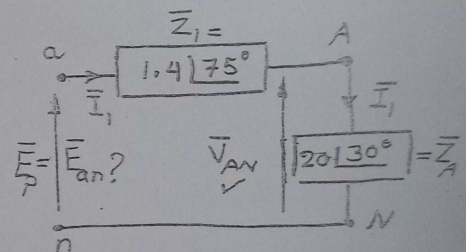


Fig. 2 1-phase (or, per-phase) circuit.

Since the given system is balanced, then use the per-phase equivalent circuit of Fig. 2.

$$\therefore V_{AB} = 4.4 \text{ kV} \quad \therefore V_{AN} = \frac{4.4}{\sqrt{3}} \text{ kV} \approx 2540 \text{ V}$$

Let $\bar{V}_{AN} = 2540 \angle 0^\circ \text{ V}$, as reference phasor, then Ohm's law gives:

$$\bar{I}_1 = \frac{2540 \angle 0^\circ}{20 \angle 30^\circ} = 127 \angle -30^\circ \text{ A, and KVL, yields:}$$

$$\bar{E}_{an} = \bar{V}_{AN} + \bar{I}_1 \bar{Z}_1 = 2540 \angle 0^\circ + (127 \angle -30^\circ)(1.4 \angle 75^\circ) = 2670 \angle 2.7^\circ \text{ V}$$

(page 1)


Example (2)

Find ① $\bar{I}_{12}, \bar{I}_{23}, \bar{I}_{31}$

② $\bar{I}_1, \bar{I}_2, \bar{I}_3$

③ P, Q, S .

④ Complete phasor diagram.

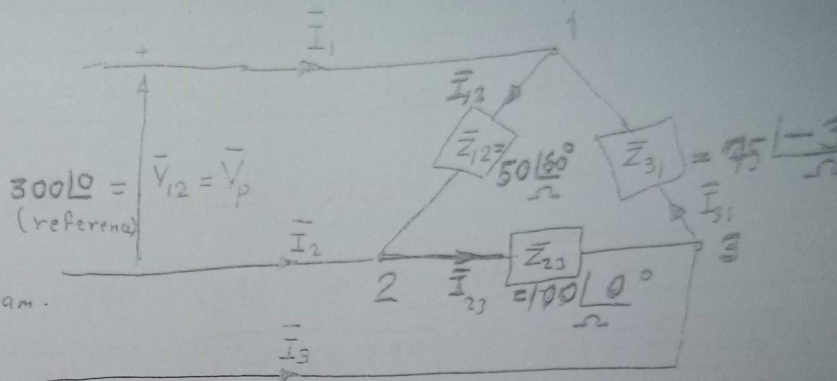

Solution: For +ve phase sequence, 123 , let

$$\bar{V}_{12} = 300 \angle 0^\circ \text{ as reference phasor,}$$

$$\therefore \bar{V}_{23} = 300 \angle -120^\circ,$$

$$\bar{V}_{31} = 300 \angle 120^\circ$$

Phase currents:

$$\bar{I}_{12} = \frac{\bar{V}_{12}}{\bar{Z}_{12}} = 6 \angle -60^\circ$$

$$\bar{I}_{23} = \frac{\bar{V}_{23}}{\bar{Z}_{23}} = 3 \angle -120^\circ$$

$$\bar{I}_{31} = \frac{\bar{V}_{31}}{\bar{Z}_{31}} = 4 \angle 150^\circ$$

Line currents:

$$\bar{I}_1 = \bar{I}_{12} - \bar{I}_{31} = 9.67 \angle -48^\circ$$

$$\bar{I}_2 = \bar{I}_{23} - \bar{I}_{12} = 5.2 \angle 150^\circ$$

$$\bar{I}_3 = \bar{I}_{31} - \bar{I}_{23} = 5 \angle 113^\circ$$

Complex power $\tilde{S} = P + jQ$

$$\tilde{S} = \sum V_p I_p^* = \bar{V}_{12} \bar{I}_{12}^* + \bar{V}_{23} \bar{I}_{23}^* + \bar{V}_{31} \bar{I}_{31}^*$$


$$= (300 \angle 0^\circ)(6 \angle 60^\circ) + (300 \angle -120^\circ)(3 \angle 120^\circ) + (300 \angle 120^\circ)(4 \angle 210^\circ)$$

$$\therefore \tilde{S} = 2840 + j960 \text{ (VA)} \Rightarrow S = \sqrt{P^2 + Q^2} = 2997 \text{ VA}$$

$$\therefore P = 2840 \text{ W}, \quad Q = 960 \text{ VAR}$$

$$\text{N.B. } \begin{aligned} P &= \sum I_p^2 R \\ Q &= \sum I_p^2 X \end{aligned}$$


phasor diagram

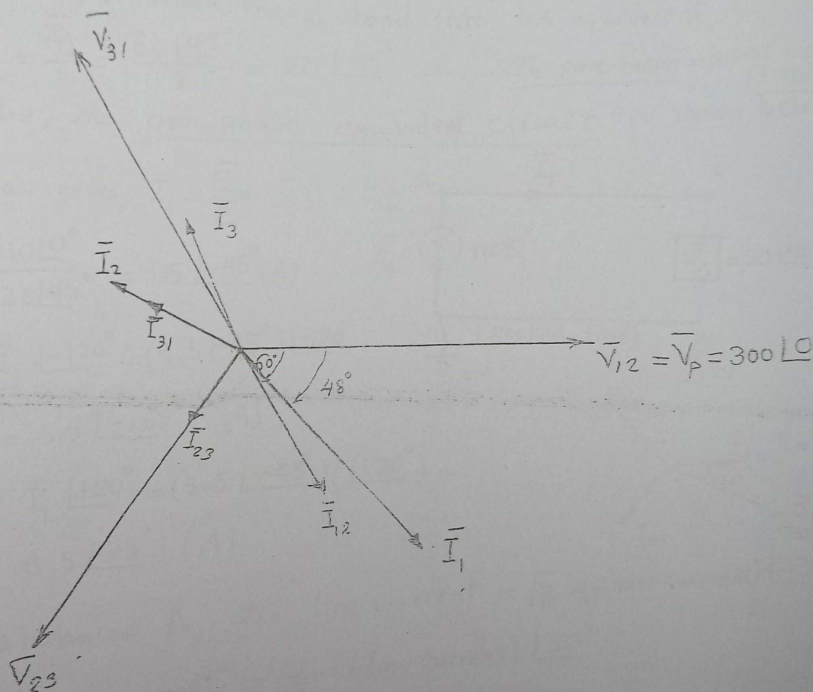

Note that the phase currents and line currents form unbalanced sets;

In the balanced 3-phase system shown in fig. 1, find:

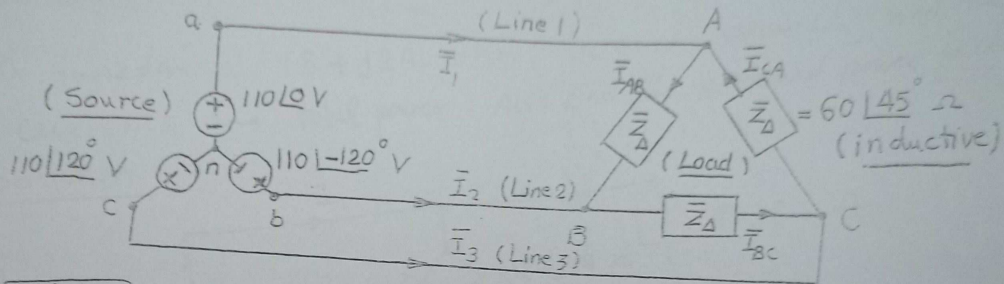- (1)- The line currents. [The phase sequence is abc (or, ABC, or 123)].
- (2)- The currents in each phase of the load.
- (3)- The complex power delivered to the load.
- (4)- The power factor of the system



Solution (1) First, transform the Δ -load into an equivalent λ :

$$\bar{Z}_\lambda = \frac{\bar{Z}_\Delta}{3} = \frac{60 \angle 45^\circ}{3} = 20 \angle 45^\circ \Omega. \therefore \text{The power factor} = \cos 45^\circ = 0.707 \text{ (lagging)}.$$

Therefore, the per-phase equivalent circuit is shown below:

∴ Ohm's law gives, $\bar{I}_1 = \frac{\bar{E}_a}{\bar{Z}_\lambda}$



$$\therefore \bar{I}_1 = \frac{110 \angle 0^\circ}{20 \angle 45^\circ} = 5.5 \angle -45^\circ \text{ (A)}$$

$$\therefore \bar{I}_2 = \bar{I}_1 \angle -120^\circ = (5.5 \angle -45^\circ) \angle -120^\circ$$

$$\therefore \bar{I}_2 = 5.5 \angle -165^\circ \text{ (A)}$$

And, $\bar{I}_3 = \bar{I}_1 \angle 120^\circ = (5.5 \angle -45^\circ) \angle 120^\circ$
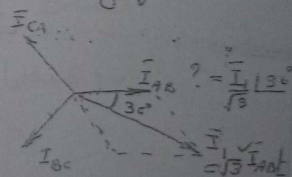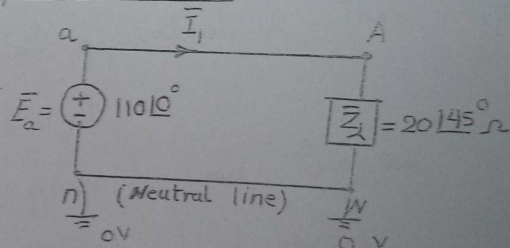
$$\therefore \bar{I}_3 = 5.5 \angle 75^\circ \text{ (A)}$$



(2) In a balanced Δ , the line current $= \sqrt{3} \times (\text{phase current}) \angle -30^\circ$

$$\therefore \text{Phase current} = \frac{1}{\sqrt{3}} \times (\text{line current}) \angle 30^\circ$$

$$\therefore \bar{I}_{AB} = \frac{\bar{I}_1}{\sqrt{3}} \angle 30^\circ = \frac{(5.5 \angle -45^\circ) \angle 30^\circ}{\sqrt{3}} = 3.18 \angle -15^\circ \text{ (A)}$$

$$\therefore \bar{I}_{BC} = \bar{I}_{AB} \angle -120^\circ = (3.18 \angle -15^\circ) \angle -120^\circ = 3.18 \angle -135^\circ \text{ (A)}$$


$$\bar{I}_{CA} = \bar{I}_{AB} \angle 120^\circ = (3.18 \angle -15^\circ) \angle 120^\circ = 3.18 \angle 105^\circ \text{ (A)}$$

(3) Total 3-phase complex power $\bar{S} = 3 I_1^2 \bar{Z}_\lambda = 3 (5.5)^2 (20 \angle 45^\circ) = 1815 \angle 45^\circ \text{ (VA)}$ (page 5)

Example(6) Parallel loads:

A 3-phase, 3-wire supply of 173 V supplies two balanced 3-phase loads; one Y-connected with each branch impedance $8 + j8 \text{ ohm}$, and the other Δ -connected with impedance $18 + j24 \text{ ohm}$ in each branch. Find the total line currents and total power. Also find the combined power factor.


Solution :

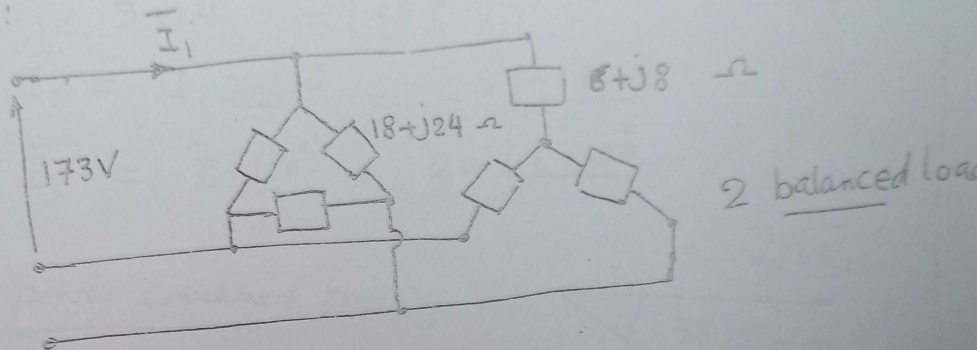


First, Convert the Δ -load to an equivalent λ . Then use the per phase equivalent circuit.

The Equivalent Y-load of the given Δ -load, has an impedance $\frac{18 + j24}{3} = 6 + j8 \text{ ohms}$, in each branch.

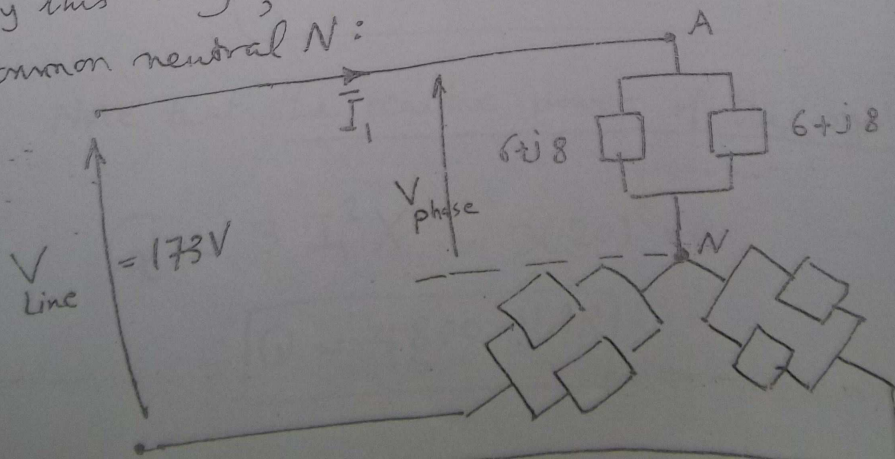By this way, we have two parallel λ -loads, with a common neutral N:



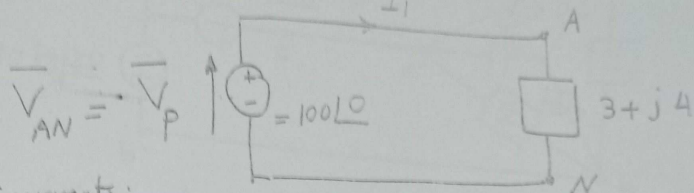Then use the per phase equivalent circuit to find the line current, with $V_{\text{phase}} = \frac{173}{\sqrt{3}} \approx 100 \text{ V}$. Let $\bar{V}_p = 100 \angle 0^\circ$



Line Currents:

$$\therefore \bar{I}_1 = \frac{\bar{V}_p}{3 + j4} = \frac{100 \angle 0^\circ}{5 \angle 53.1^\circ} = 20 \angle -53.13^\circ$$


$$\bar{I}_2 = \bar{I}_1 \angle -120^\circ = 20 \angle -173.13^\circ$$

$$\bar{I}_3 = \bar{I}_1 \angle 120^\circ = 20 \angle 66.87^\circ$$

The total power consumed by the two loads is

$$P = 3 I_1^2 \times 3 = 3(20)^2 \times 3$$
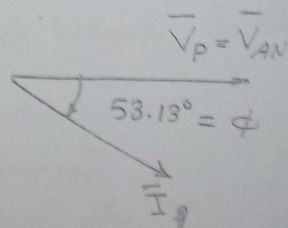
$$\therefore \boxed{P = 3600 \text{ Watt}}$$



The power factor of the system is

$$\boxed{\cos \phi = \cos 53.13 = 0.6} \quad (\text{lagging P.F.})$$

Note that the reactive power of the system is

$$Q = 3 I_1^2 X = 3(20)^2 \times 4$$

$$\therefore \boxed{Q = 4800 \text{ VAR}}$$

and the line currents and the total power consumed by the load in the system shown in Fig. 3. Assume that: $f = 400 \text{ Hz}$, $R = 100 \Omega$, $L = 100 \text{ mH}$, $C = 0.47 \mu\text{F}$, and $\bar{Z} = 50 \angle 37^\circ \Omega$.

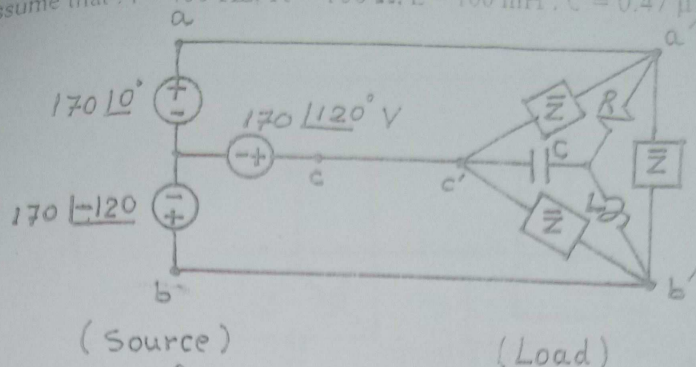


Fig. 3

Solution: $\omega = 2\pi f = 800\pi \text{ rad/s}$

$$\bar{Z}_C = -j \frac{1}{\omega C} = -j 846.6 \Omega, \quad \bar{Z}_L = j\omega L = j 251.33 \Omega$$

The best way to solve this problem is to transform the unbalanced Δ into an equivalent Δ , as shown in Fig. (a). Then, replace each pair of parallel branches by a single branch to obtain an equivalent Δ , as shown in Fig. (b).

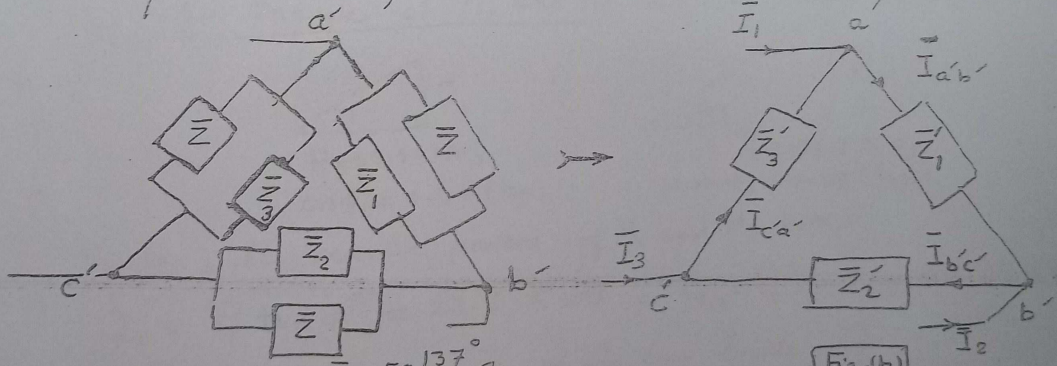


Fig. (a): $\bar{Z}_1 = 2209.46 \angle -15.6^\circ$, $\bar{Z}_2 = 261 \angle 74.4^\circ$, $\bar{Z}_3 = 879.1 \angle 74.4^\circ$

Fig. (b): $\bar{Z}_1' = 48.2 \angle 142.8^\circ$, $\bar{Z}_2' = 49.3 \angle 136^\circ$, $\bar{Z}_3' = 52.3 \angle 135^\circ$

The 3 line voltages are $\bar{V}_{ab} = 170\sqrt{3} \angle 30^\circ$, $\bar{V}_{bc} = 170\sqrt{3} \angle -90^\circ$, and $\bar{V}_{ca} = 170\sqrt{3} \angle 150^\circ$. Therefore, the phase currents in Fig. (b) are:

$$\bar{I}_{a'b'} = \frac{\bar{V}_{a'b'}}{\bar{Z}_1'} = 6.82 \angle -12.8^\circ, \quad \bar{I}_{b'c'} = 6 \angle -126^\circ, \quad \bar{I}_{c'a'} = 5.6 \angle 115^\circ$$

The line currents are: $\bar{I}_1 = \bar{I}_{a'b'} - \bar{I}_{c'a'} = 11.2 \angle -36^\circ$, $\bar{I}_2 = 10.7 \angle -161^\circ$, $\bar{I}_3 = 10 \angle 83.3^\circ$. Therefore, $P_{\text{load}} = \text{Real part of } [\bar{I}_{a'b'}^2 \bar{Z}_1' + \bar{I}_{b'c'}^2 \bar{Z}_2' + \bar{I}_{c'a'}^2 \bar{Z}_3']$

Or, $P_{\text{load}} = 1474.3 + 1435.8 + 1343.5 = 4253.6 \text{ Watt}$


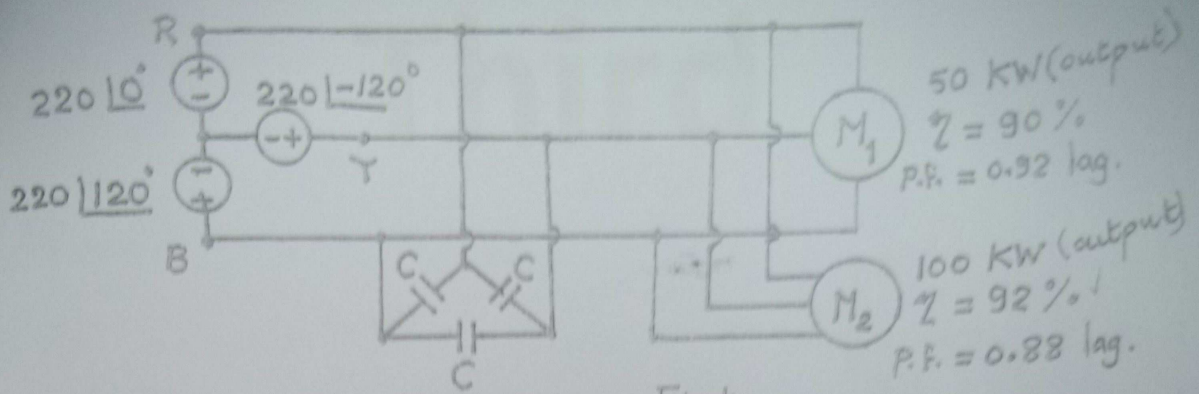
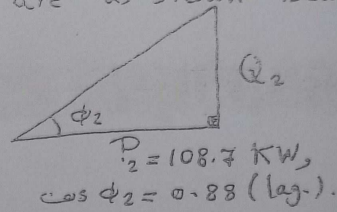


Fig. 4

Solution: First determine the input power of the two loads M_1 and M_2 , using the relation: $\eta = \frac{P_{\text{output}}}{P_{\text{input}}}$

\therefore For M_1, M_2 : $P_1 = \frac{50}{0.9} = 55.56 \text{ kW}$, $P_2 = \frac{100}{0.92} = 108.7 \text{ kW}$

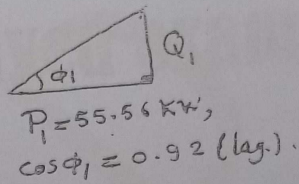The power triangles of M_1 and M_2 are as shown below:



Therefore, the reactive powers of M_1 and M_2 are:

$Q_1 = P_1 \tan \phi_1 = 23.7 \text{ KVAR}$, $Q_2 = P_2 \tan \phi_2 = 58.67 \text{ KVAR}$

The total reactive power of the two loads is

$Q = Q_1 + Q_2 = 82.37 \text{ KVAR}$

To increase the power factor of the system to unity, the reactive power of the 3 capacitors must equal to

$Q = 82.37 \text{ KVAR}$. Consequently, the reactive power of each capacitor is $Q_c = \frac{Q}{3} = 27.46 \text{ KVAR}$.

The capacitance is: $C = \frac{Q_c}{\omega V_c^2}$, where $\omega = 2\pi f$, and

$V_c = 220\sqrt{3} \text{ (Volt)}$. $\therefore C = \frac{27.46 \times 10^3}{2\pi \times 50 \times (220\sqrt{3})^2}$

the system shown in fig. 4, determine the value of C to raise the power factor to 1. The supply frequency is 50 Hz. (M_1 and M_2 are two motors).


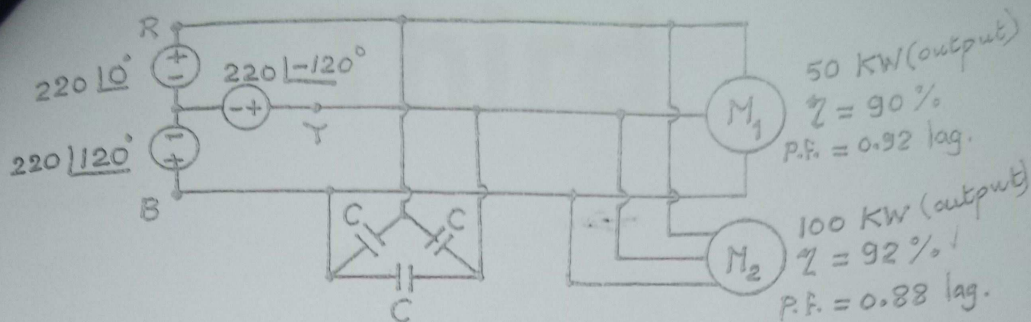
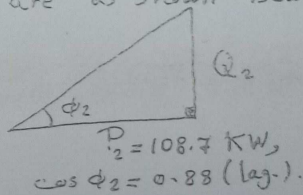


Fig. 4

Solution: First determine the input power of the two loads M_1 and M_2 , using the relation: $\eta = \frac{P_{\text{output}}}{P_{\text{input}}}$

$$\therefore \text{For } M_1, M_2: P_1 = \frac{50}{0.9} = 55.56 \text{ KW}, P_2 = \frac{100}{0.92} = 108.7 \text{ KW}$$

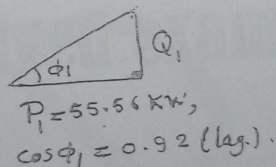The power triangles of M_1 and M_2 are as shown below:



Therefore, the reactive powers of M_1 and M_2 are:

$$Q_1 = P_1 \tan \phi_1 = 23.7 \text{ KVAR}, Q_2 = P_2 \tan \phi_2 = 58.67 \text{ KVAR.}$$

The total reactive power of the two loads is

$$Q = Q_1 + Q_2 = 82.37 \text{ KVAR}$$

To increase the power factor of the system to unity, the reactive power of the 3 capacitors must equal to

$$Q = 82.37 \text{ KVAR. Consequently, the reactive power of each capacitor is } Q_c = \frac{Q}{3} = 27.46 \text{ KVAR.}$$

The capacitance is: $C = \frac{Q_c}{\omega V_c^2}$, where $\omega = 2\pi f$, and

$$V_c = 220\sqrt{3} \text{ (Volt).} \therefore C = \frac{27.46 \times 10^3}{2\pi \times 50 (220\sqrt{3})^2}$$

Third

Solved examples impedance

1. Consider the phase shifting circuit shown in Fig.1. The source frequency is 1000 Hz. The values of R and C are always adjusted so that the magnitude of their total impedance is 5000Ω. Determine the values of R and C which produces a phase shift of 30° between $V_o(t)$ and $V_s(t)$. Show whether $V_o(t)$ lags or leads $V_s(t)$.


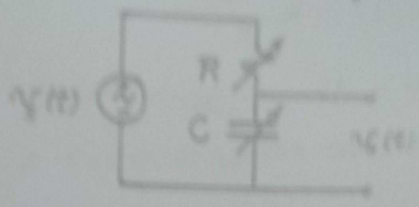


Fig.1

The impedance of the circuit is

$$\underline{Z} = R - jX_C$$

$$|\underline{Z}| = Z = \sqrt{R^2 + X_C^2} = 5000 \quad \dots \quad (1)$$

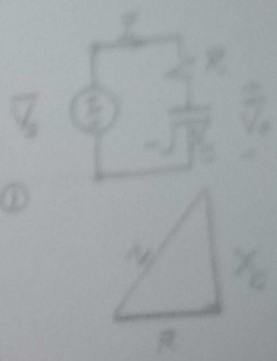

From Fig. 1 :

$$\frac{\underline{V}_o}{\underline{V}_s} = \frac{\underline{I}(-jX_C)}{\underline{I}(R - jX_C)} = \frac{X_C \angle -90^\circ}{\sqrt{R^2 + X_C^2} \angle -\tan^{-1} \frac{X_C}{R}}$$

$$\frac{\underline{V}_o}{\underline{V}_s} = \frac{X_C}{\sqrt{R^2 + X_C^2}} \angle \left[\tan^{-1} \left(\frac{X_C}{R} \right) - 90^\circ \right]$$

$$\therefore \text{phase shift} = \tan^{-1} \left(\frac{X_C}{R} \right) - 90^\circ = -30^\circ$$

$$\therefore \tan^{-1} \left(\frac{X_C}{R} \right) = 60^\circ$$

$$\therefore X_C = \sqrt{3} R \quad \dots \quad (2)$$

Solving (1) and (2)



$$\boxed{R = 2500 \, \Omega}, \text{ and } X_C = \frac{1}{\omega C} = 4930.13 \, \Omega$$

$$\omega = 2\pi \times 1000 \, \text{rad/s}$$

$$\therefore \boxed{C = 0.037 \, \mu\text{F}}$$

Another simple solution, using phasor diagram and impedance triangle:

Impedance triangle

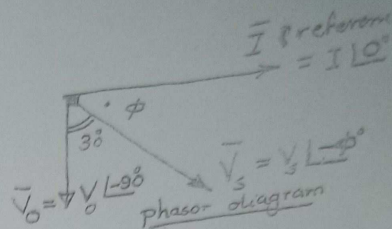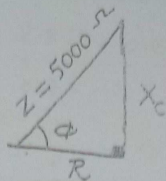

From the phasor diagram, $\phi = 90^\circ - 30^\circ = 60^\circ$

$$\therefore R = Z \cos \phi = 5000 \cos 60^\circ = 2500 \Omega,$$

$$X_c = Z \sin \phi = 5000 \sin 60^\circ = 5000 \times \frac{\sqrt{3}}{2} = 4330.13 \Omega, \text{ as}$$

before. N.B. \bar{V}_0 lags \bar{V}_3 by 30° .

2. In the circuit of Fig.2, find:

a- The value of R if \bar{I} is to lag behind \bar{V}_s by 90° .

b- The value of R which will draw maximum power from the circuit.

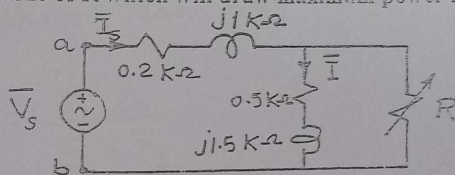


Fig.2

2) The impedance seen by the source is:

$$\bar{Z}_{ab} = \bar{Z}_1 + \frac{R \bar{Z}_2}{R + \bar{Z}_2} \text{ k}\Omega, \text{ where } \bar{Z}_1 = 0.2 + j1, \bar{Z}_2 = 0.5 + j1.5$$

$$\therefore \bar{I}_s = \frac{\bar{V}_s}{\bar{Z}_{ab}} = \frac{V(R + \bar{Z}_2)}{\bar{Z}_1 \bar{Z}_2 + R(\bar{Z}_1 + \bar{Z}_2)}, \text{ where } \bar{V}_s = V \angle 0$$

Using the current divider,

$$\therefore \bar{I} = \bar{I}_s \frac{R}{R + \bar{Z}_2} = \frac{VR}{\bar{Z}_1 \bar{Z}_2 + R(\bar{Z}_1 + \bar{Z}_2)}$$

$$\therefore \bar{I} = \frac{VR}{(0.7R - 1.4) + j(2.5R + 0.8)}$$

N.B. from the last eqⁿ \bar{I} (as $\bar{V}_s = V \angle 0$)
denominator equals zero, i.e., $-2 -$
 $(0.7R - 1.4) = 0 \Rightarrow R = 4 \text{ k}$

$$\angle \bar{I} = -\tan^{-1} \left(\frac{2.5R + 0.8}{0.7R - 1.4} \right) = -90^\circ$$

$$\therefore \tan \left(\frac{2.5R + 0.8}{0.7R - 1.4} \right) = \infty$$

$$\therefore 0.7R - 1.4 = 0$$


$$\therefore \boxed{R = 2 \text{ K}\Omega}$$

(b) Using Thevenin's theorem, the value of R for maximum power transfer is:

$$R = \sqrt{R_T^2 + X_T^2} = |\bar{Z}_T|$$


The value of \bar{Z}_T is determined by short circuiting the independent source \bar{V}_S , and then finding the impedance seen by the load:
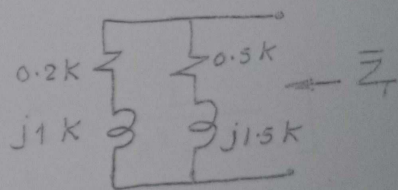
$$\therefore \bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$$



$$\therefore \bar{Z}_T = 0.1513 + j0.602 \text{ K}\Omega$$
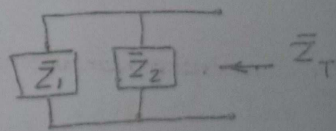
$$\therefore \boxed{R = 0.62 \text{ K}\Omega}$$



Note that, \bar{Z}_T may be determined by another 2 methods:

$$\bar{Z}_T = \frac{\bar{V}_T}{\bar{I}_{sc}}$$

$$\text{or, } \bar{Z}_T = \frac{\bar{V}_{ex}}{\bar{I}_{ex}}$$

from the source is minimum, and find the value of that current. Sketch a phasor diagram representing the source voltage and various currents.

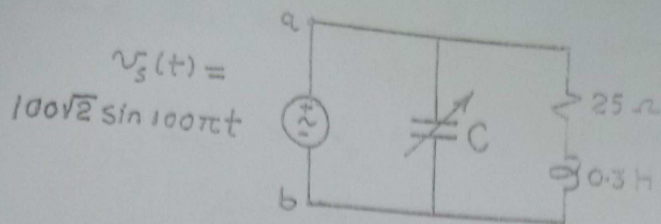


Fig. 3

The circuit in the phasor domain is shown in Fig. (1-3)

∴ The admittance seen by the source is :

$$\bar{Y}_{ab} = \frac{1}{-jX_C} + \frac{1}{R + jX_L}$$

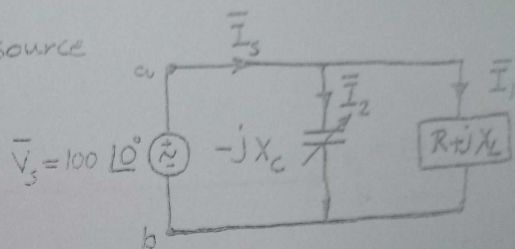


Fig. (1-3)

with $X_C = \frac{1}{\omega C}$, $X_L = \omega L$,

$\omega = 100\pi$ r/s

$$\bar{Y}_{ab} = \frac{R}{(R^2 + \omega^2 L^2)} + j\omega \left[C - \frac{L}{(R^2 + \omega^2 L^2)} \right]$$

Therefore, the supply current is minimum when \bar{Y}_{ab} is minimum, i.e., \bar{Z}_{ab} is maximum.

∴ \bar{Y}_{ab} is minimum if the imaginary part of \bar{Y}_{ab} equal zero. That is, the source current is in phase with \bar{V}_s .

$$C = \frac{L}{R^2 + \omega^2 L^2} = \frac{0.3}{25^2 + (100\pi)^2 (0.3)^2}$$

$$\therefore \boxed{C = 31.583 \mu F}$$

∴ The minimum value of \bar{Y}_{ab} is :


$$Y_{min} = \frac{R}{R^2 + \omega^2 L^2} = \frac{25}{25^2 + (100\pi)^2 (0.3)^2} = 2631.92 \mu S$$

and the minimum value of source current is

$$I_{min} = V_s \cdot Y_{min} = 100 \times 2631.92 \times 10^{-6}$$

$$\therefore \boxed{I_{min} = 0.2632 \text{ A}}$$

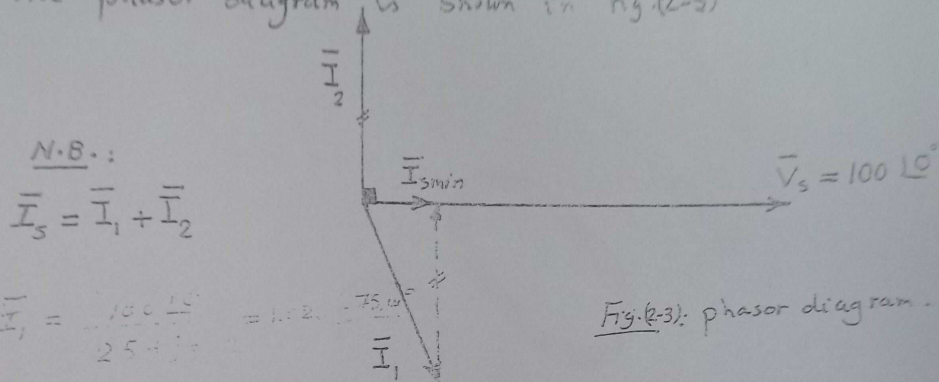The phasor diagram is shown in Fig. (2-3)



Another simple solution for question 3:

From the phasor diagram, it is clear that the source current is minimum when the source power factor is unity. To achieve this objective, the reactive power of the parallel capacitor must equal to the load reactive power (here the load is formed of R, L), as shown in Fig. (3-3); where,

$$P = I_1^2 R = \frac{V_s^2}{(R^2 + \omega^2 L^2)} \cdot R = 26.3 \text{ W}$$

$$\therefore Q = P \tan \phi, \quad \phi = \tan^{-1} \frac{X_L}{R}$$

$$\therefore Q = 99.1 \text{ VAR} = Q_C = V_s^2 \cdot \omega C$$

$$\therefore \boxed{C \approx 31.5 \mu F}$$

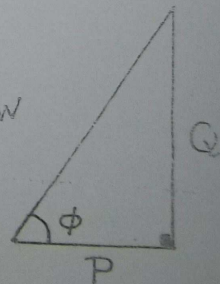


Fig. (3-3): power triangle

Fourth

Circuit analysis solved with all
methods

Q. In the circuit shown in Fig. 1, find the value of i using

- [1] Kirchhoff's laws
- [2] Nodal analysis
- [3] Mesh analysis
- [4] Source transformation
- [5] Superposition
- [6] Thevenin's method

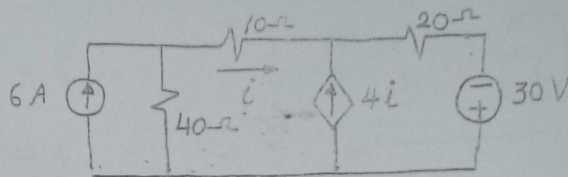


Fig. 1

Solution: [1] By Kirchhoff's laws; (KCL and KVL):

First, distribute the currents in different branches, as shown in Fig. 2.

Then, apply KVL around the loop abcd (Σ $V_{rise} = 0$)

$$30 = 10i + 20(5i) - 40(6-i) \quad \therefore i = 1.8 \text{ A}$$

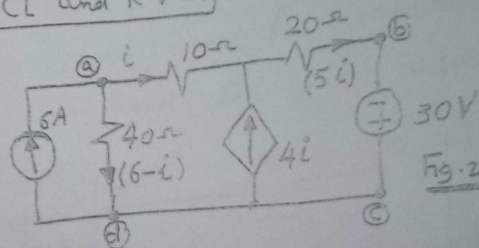


Fig. 2

[2] Using nodal analysis: select lower node as reference (0). Then, write the voltages of the remaining nodes, as shown in Fig. Now, you have 3 unknowns (i, V_1, V_2).

Node 1: $-6 + \frac{V_1 - 0}{40} + i = 0$

$$\therefore V_1 = 240 - 40i \quad \text{①}$$

Node 2: $-i - 4i + \frac{V_2 - (-30)}{20} = 0$

$$V_2 = 100i - 30 \quad \text{②}$$

Constraint equation: $V_1 - V_2 = 10i$ (Ohm's law) ... ③

Solving ①, ② and ③

$$\therefore i = 1.8 \text{ A}$$

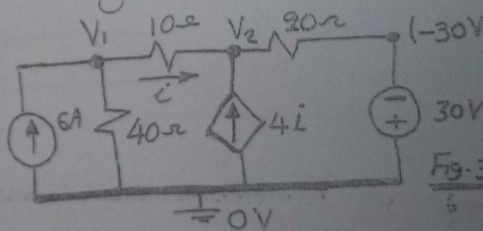



Fig. 3

3) Using mesh analysis: Assume the 3 mesh-currents I_1, I_2 and I_3 as shown in Fig.4. Now, you have 4 unknowns (I_1, I_2, I_3 and i). The 3 mesh-equations are:

Mesh 1: $I_1 = 6 \dots \dots \dots \textcircled{1}$


Mesh 2: $I_2 = i \dots \dots \dots \textcircled{2}$

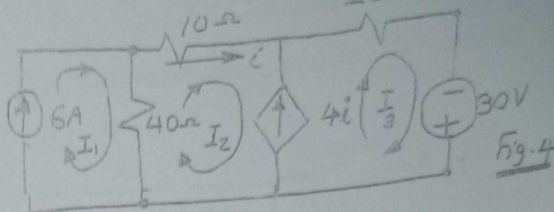Mesh 3: $I_3 - I_2 = 4i \dots \dots \textcircled{3}$



To write the 4th equation, imagine that you have removed all current sources; by this way you have the loop abcd, shown in Fig.5.

Apply KVL around this loop, you get:

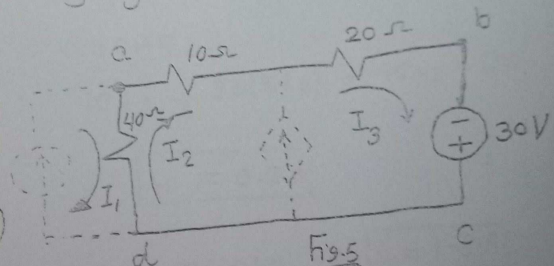

$$30 = 10 I_2 + 20 I_3 + 40(I_2 - I_1)$$

$$5 I_2 - 4 I_1 + 2 I_3 = 3 \dots \dots \textcircled{4}$$

Solve $\textcircled{1} \rightarrow \textcircled{4}$, you obtain: $i = 1.8 \text{ A}$

4) By source transformation:

First transform the $(30 \text{ V}, 20 \Omega)$ to an equivalent current source $\frac{30}{20} = 1.5 \text{ A}$, in parallel with 20Ω , as shown in Fig.6. Then combine the $\parallel (4i)$ and 1.5 A sources into a single source $(4i - 1.5) \text{ A}$, as shown in Fig.7. Finally, transform the $(6 \text{ A}, 40 \Omega)$ and $[(4i - 1.5) \text{ A}, 20 \Omega]$ to equivalent $(240 \text{ V}, 40 \Omega)$ and $[(80i - 30) \text{ V}, 20 \Omega]$, Fig.8.


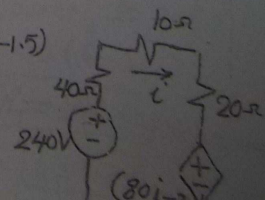
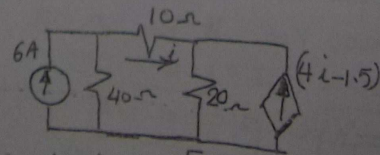
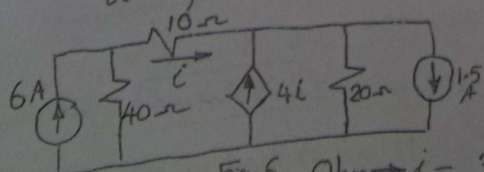


Fig.6: Ohm $\rightarrow i = \frac{240 - (80i - 30)}{20} \Rightarrow i = 1.8 \text{ A}$

① 6A-ON, and 30V-OFF

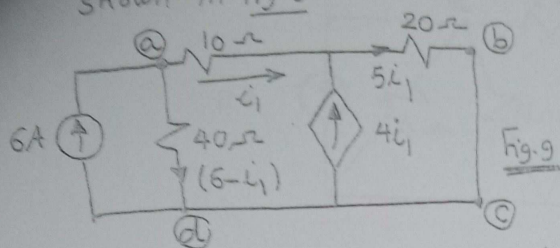The corresponding circuit is shown in Fig. 9:




∴ To find i_1 , apply KVL around the loop $\textcircled{a} \textcircled{b} \textcircled{c} \textcircled{d} \textcircled{a}$:

$$\therefore 10i_1 + 5i_1(20) - 40(6 - i_1) = 0$$

$$\therefore \boxed{i_1 = 1.6 \text{ A}}$$

② 30V-ON, and 6A OFF

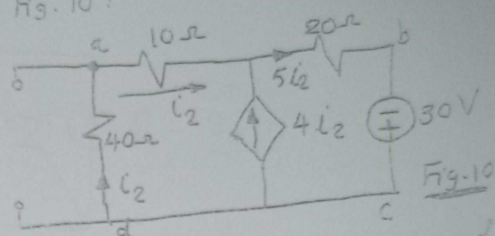The corresponding circuit is shown in Fig. 10:



To find i_2 , apply KVL around abcd :

$$10i_2 + 20(5i_2) + 40i_2 = 30$$


$$\therefore \boxed{i_2 = 0.2 \text{ A}}$$

Finally, superpose i_1 and i_2 , i.e., $i = i_1 + i_2 \Rightarrow \boxed{i = 1.8 \text{ A}}$


6 Using Thevenin's Theorem:

To find i through 10Ω , Thevenin's equivalent circuit is shown in Fig. 11, where:

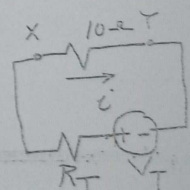$V_T =$ open-circuit voltage between X and Y,
 $R_T = \frac{V_T}{I_{s.c.}}$, where $I_{s.c.} =$ short-circuit current through XY.




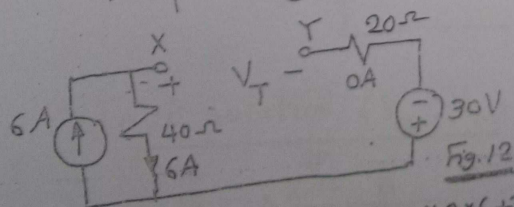V_T and $I_{s.c.}$ are determined using Fig. 1, as in Figs. 12 and 13,



$$V_T = V_{40\Omega} + 30 = 40 \times 6 + 30$$

$$\boxed{V_T = 270 \text{ V}}$$

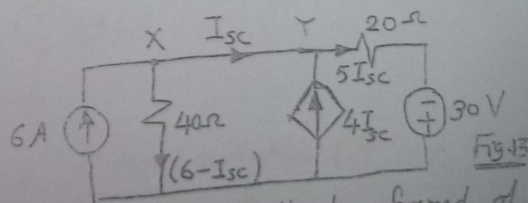

Apply KVL around the loop formed of 20Ω , 40Ω and the 30V source, to get:


$$30 = 20(5I_{sc}) - 40(6 - I_{sc})$$

$$\therefore \boxed{I_{sc} = \frac{27}{14} \text{ A}} \quad \therefore \boxed{R_T = 140\Omega}$$

Now, go back to Fig. 11, $\therefore i = \frac{V_T}{(R_T + 10)} = \frac{270}{(140 + 10)} \Rightarrow \boxed{i = 1.8 \text{ A}}$

solution of mid-term exam.


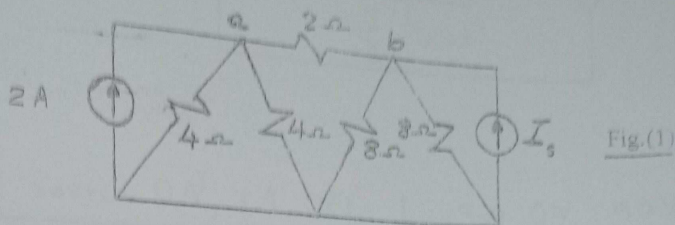
1. For the circuit shown in fig.(1), it is desired that voltage drop between a and b is equal to 3 volts by adjusting the value of (I_s). Find I_s to achieve the desired value of voltage drop.




The problem has 2 possible solutions, and can be solved using source transformation:

$$\therefore 4 \parallel 4 \rightarrow 2\Omega, \quad 8 \parallel 8 \rightarrow 4\Omega$$


\therefore The circuit is reduced to:

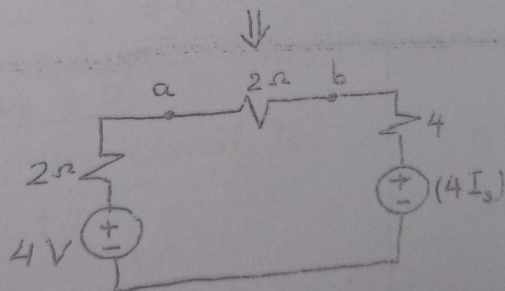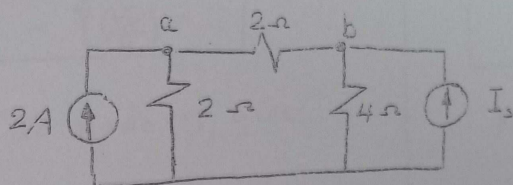

First solution ($V_a > V_b$):

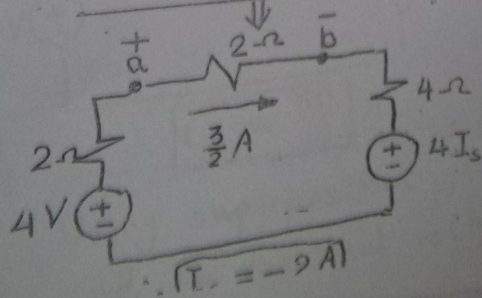

Second solution ($V_b > V_a$):

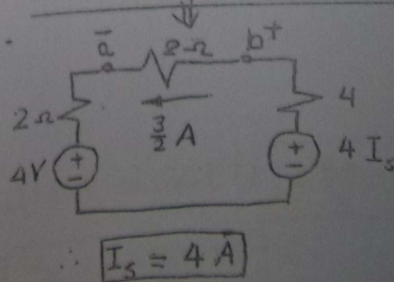

superposition theorem to find V_x and i_x in the circuit of Fig. (2)


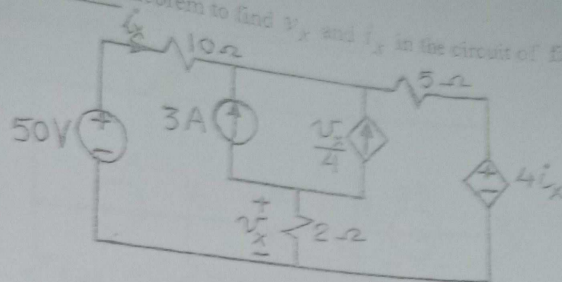


Fig. (2)

50-V source ON, 3A OFF:

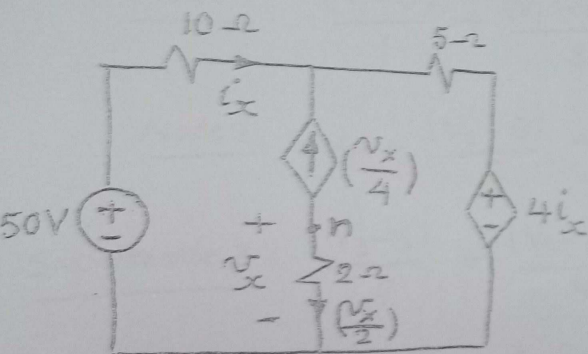


∴ KCL, at node n , gives:

$$\frac{V_x}{4} + \frac{V_x}{2} = 0$$


$$\therefore \boxed{V_x = 0}$$

Therefore, the circuit is reduced to

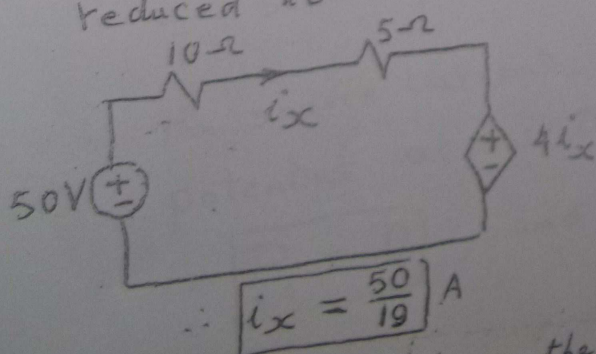

$$\therefore \boxed{i_x = \frac{50}{19} \text{ A}}$$

3A ON, 50V OFF:

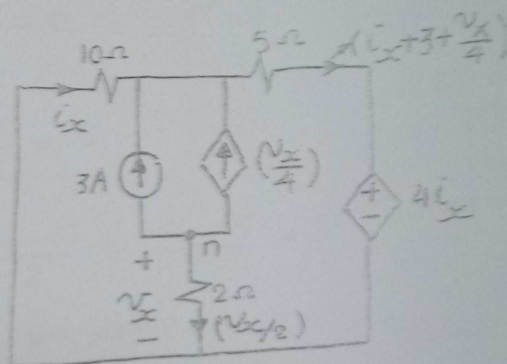

∴ KCL, at node n , gives:

$$3 + \frac{V_x}{4} + \frac{V_x}{2} = 0$$


$$\boxed{V_x = -4 \text{ V}}$$

KVL, around outer loop, gives:

$$10i_x + 5\left(i_x + 3 + \frac{V_x}{4}\right) + 4i_x = 0$$

$$\therefore \boxed{i_x = -\frac{10}{19} \text{ A}}$$

Using superposition, the resultant current $i_x = \frac{50}{19} - \frac{10}{19} = \frac{40}{19} \text{ A}$,
the resultant voltage is $V_x = 0 - 4 = -4 \text{ V}$.

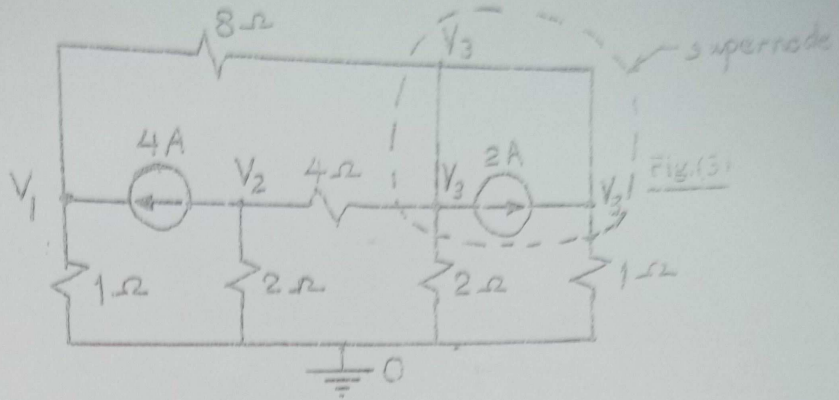

Node 1: $\frac{(V_1 - 0)}{1} + \frac{(V_1 - V_3)}{8} - 4 = 0$ (1)

Node 2: $4 + \frac{(V_2 - 0)}{2} + \frac{(V_2 - V_3)}{4} = 0$ (2)

Supernode 3: $\frac{(V_3 - V_1)}{8} + \frac{(V_3 - V_2)}{4} + \frac{(V_3 - 0)}{2} + \frac{(V_3 - 0)}{1} = 0 \dots (3)$

Solving equations 1, 2 and 3, we get:

$$\boxed{V_1 = 3.5} \text{ V ,}$$

$$\boxed{V_2 = -5.5} \text{ V , and}$$

$$\boxed{V_3 = -0.5} \text{ V .}$$

\therefore source power $P_s = V_s I_s$ (Watt), where I_s is the source current, and V_s is the difference of potential across the source.

$\therefore \boxed{P_{2A} = 0}$, and $P_{4A} = (V_1 - V_2) \times 4 = [3.5 - (-5.5)]$

$\therefore \boxed{P_{4A} = 36} \text{ W}$